

# Inter-Operation of the DS14C335 with +5V UARTs

National Semiconductor  
 Application Note 876  
 John Goldie  
 Joe Vo  
 January 1993



This application brief describes the inter-operation between the DS14C335 (+3.3V supply TIA/EIA-232 3 x 5 Driver/Receiver) and a +5V UART. The DS14C335, illustrated in Figure 1, is ideally suited for notebook and laptop computer applications which either employ one uniform +3.3V supply for all internal components or mixed +3.3V and +5V power supplies. In mixed supply applications, the DS14C335 does NOT require a +5V to +3.3V translator device between it and the UART. This application brief describes how this is accomplished.

Figure 2 illustrates a typical application where the DS14C335 provides the interface between the +5V UART

and the RS-232 port. The drivers provide translation from TTL/CMOS voltage levels on the driver input pins to RS-232 compliant driver output voltage levels ( $>|5V|$ ), while the receivers accept standard RS-232 input levels and translate them back to TTL/CMOS compatible output voltage levels.

Because this application specifies a +5V UART, care must be taken to consider the characteristics of three pins on the DS14C335. They are the:

- D<sub>IN</sub> Driver Input,
- SD Shutdown,
- R<sub>OUT</sub> Receiver Output

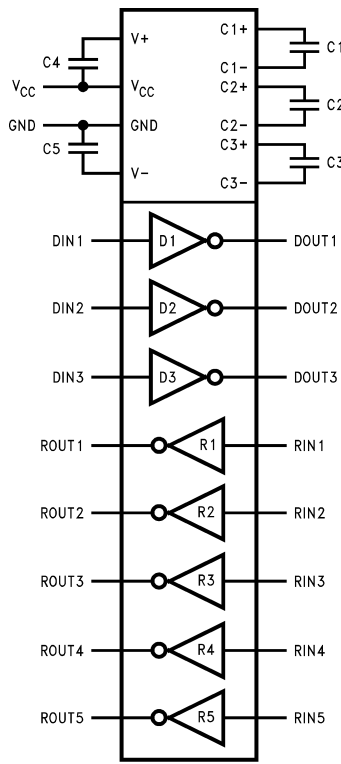


FIGURE 1. DS14C335 Functional Diagram

Inter-Operation of the DS14C335 with +5V UARTs

AN-876


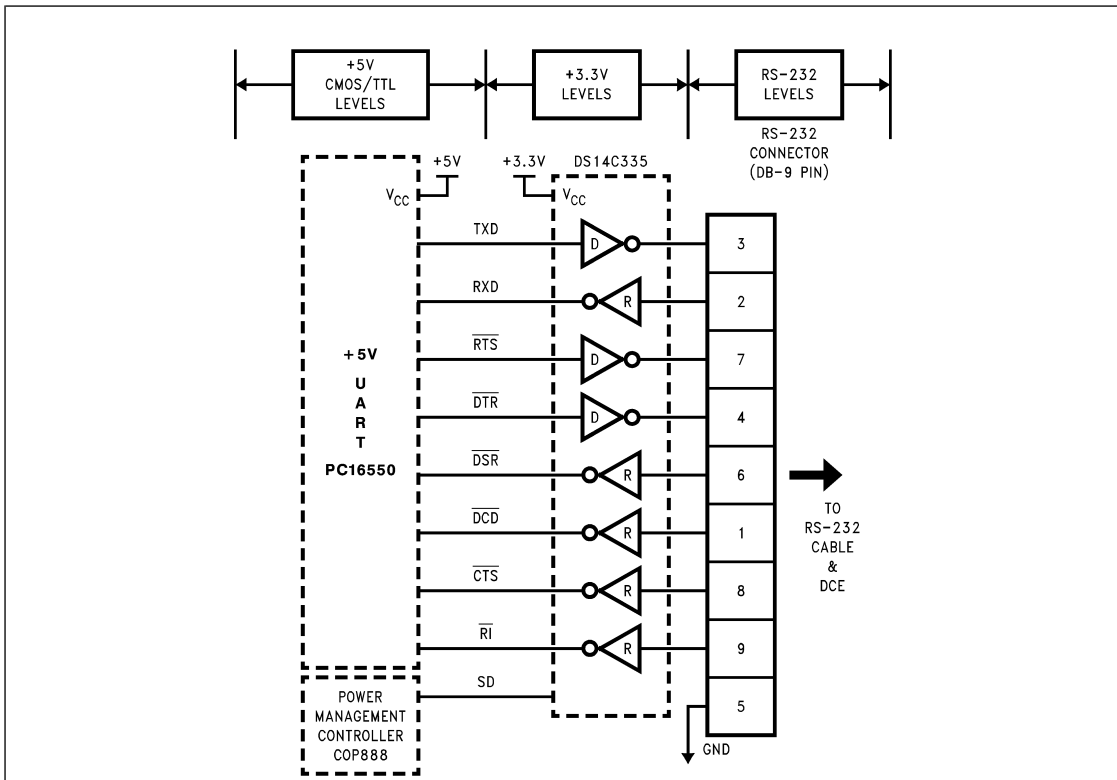


FIGURE 2. Typical Mixed Supply (3V/5V) DTE Application

Let us first examine the input structures of the  $D_{IN}$  and SD input pins, as these structures are very similar. The common circuitry is illustrated in Figure 3 and is composed of two input protection diodes (D1 and D2). In addition, a third diode (D3) exists between the  $V_{CC}$  and V+ pins and is normally reversed biased. Diode D1 is situated between the input ( $D_{IN}$  or SD) pin and GND to clamp negative input voltages. Diode D2 is situated between the input pin and the V+ pin. When the DS14C335 is active (ON), the V+ pin is typically greater than +9V. External charge pump capacitor C4, holds 6V of charge, and is referenced to the  $V_{CC}$  (+3.3V) pin. This creates a potential of greater than +9V on the V+ pin, and is used to power the driver outputs. The input pins ( $D_{IN}$  and SD) present standard input current loading to the driving device (UART) since D1 and D2 remain reversed biased between -0.3V and one diode above the V+ pin potential (typically greater than +9V).

The DS14C335 supports another unique feature that allows the CPU to disable the device to save power when RS-232 communication is not required. The DS14C335 is put into shutdown mode, by asserting the SD pin high. This disables the internal charge pump circuit, the drivers, and also 4 of the 5 receivers, dropping  $I_{CC}$  to typically 1.0  $\mu$ A (10  $\mu$ A maxi-

mum). One receiver remains active to monitor the Ring Indicator (RI) modem control line, to inform the CPU that a call is coming in from a remote site. In the shutdown mode, the charge pump is disabled, and the charge on C4 eventually drops to one diode below  $V_{CC}$ , or the input voltage, whichever is greater. If C4 has discharged to one diode below  $V_{CC}$ , and an input voltage is applied that is greater than  $V_{CC}$ , C4 will charge up to one diode below that level. However, no DC current flows between the input pin and the +3.3V supply. The  $D_{IN}$  and SD pins still present standard DC loading to the driving logic. Blocking diode D3 prevents a large DC current from flowing between the input pins and the +3.3V supply when the input pin is taken above the device's +3.3V ( $V_{CC}$ ) power supply pin. This is the classical problem that can occur when directly interfacing a +5V device to some +3.3V devices. A minimal amount of noise is coupled onto the  $V_{CC}$  (+3.3V) supply rail if the driver input pin is switched (0V to 5V) while the DS14C335 is in the shutdown mode. However, the magnitude is small, and power supply bypassing capacitors effectively filter out the noise. To prevent noise from coupling onto the  $V_{CC}$  rail to begin with, simply hold the driver inputs at a  $V_{IL}$  (voltage input low), since with a  $V_{IL}$  applied both diodes (D1 and D2) will remain off.

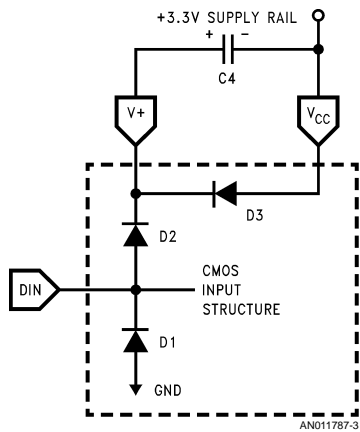

**FIGURE 3. Input Protection Circuitry**

This unique input structure allows the driver input pins and shutdown pin to accept any standard TTL/CMOS levels regardless of the DS14C335 mode (active or shutdown) or the fact that the DS14C335 is powered from a +3.3V power supply. The input pins ( $D_{IN}$  and  $SD$ ) present standard loading to the driving logic with input voltages ranging from 0V to +5.5V, in magnitude.

The last pin of concern is the receiver output ( $R_{OUT}$ ) pin. The  $R_{OUT}$  pin must have the drive capability to meet standard TTL/CMOS requirements. The  $R_{OUT} V_{OH}$  is specified to be greater than 2.4V at 1 mA. This drive capability should meet all standard TTL/CMOS requirements.

#### SUMMARY

The DS14C335's unique input structure allows the driver input ( $D_{IN}$ ) and shutdown ( $SD$ ) pins to present standard steady state input loading to the driving logic. Valid input voltages can range from -0.3V to greater than +5.5V, thereby enabling the device to be driven by a +5V UART in applications that employ mixed power supplies. The high drive capability of the receiver output meets the requirements of +5V logic levels, or CMOS compliant JEDEC +3.3V levels. These features make the DS14C335 the optimal single chip solution for RS-232 serial ports in +3.3V/+5V or pure +3.3V power supply laptop and notebook computer applications.

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
Americas  
Tel: 1-800-272-9959  
Fax: 1-800-737-7018  
Email: support@nsc.com

[www.national.com](http://www.national.com)

**National Semiconductor Europe**  
Fax: +49 (0) 1 80-530 85 86  
Email: europe.support@nsc.com  
Deutsch Tel: +49 (0) 1 80-530 85 85  
English Tel: +49 (0) 1 80-532 78 32  
Français Tel: +49 (0) 1 80-532 93 58  
Italiano Tel: +49 (0) 1 80-534 16 80

**National Semiconductor Asia Pacific Customer Response Group**  
Tel: 65-2544466  
Fax: 65-2504466  
Email: sea.support@nsc.com

**National Semiconductor Japan Ltd.**  
Tel: 81-3-5620-6175  
Fax: 81-3-5620-6179